


Switching Theory & Logic Design Laboratory
CSE Department, IIT Kharagpur
Spring Semester 2023-24

Module 1 : Combinational Logic Circuits

Assignment 4:

Design and test a 1-bit ALU using only logic gates (No MUX) as per the given specifications, supporting the following functions :

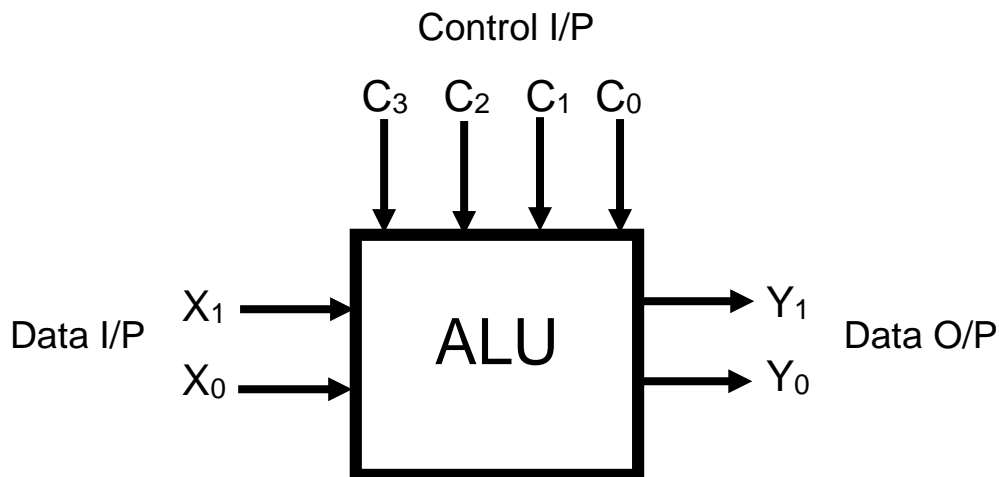Logical : AND, OR, NAND, NOR, XOR, EQUIVALENCE.
Arithmetic : ADD, SUBTRACT.



- If $C_3 = 1$: Arithmetic or If $C_3 = 0$: Logical
- If $C_3 = 1$ and If $C_2 = 1$: ADD ($Y_0 = \text{Sum}$, $Y_1 = \text{Carry out}$) or
If $C_2 = 0$: SUB ($Y_0 = \text{Sub}$, $Y_1 = \text{Borrow}$)
- If $C_3 = 0$ then $C_2 C_1 C_0$ = Logical operation (Output = Y_0)

(1 day)